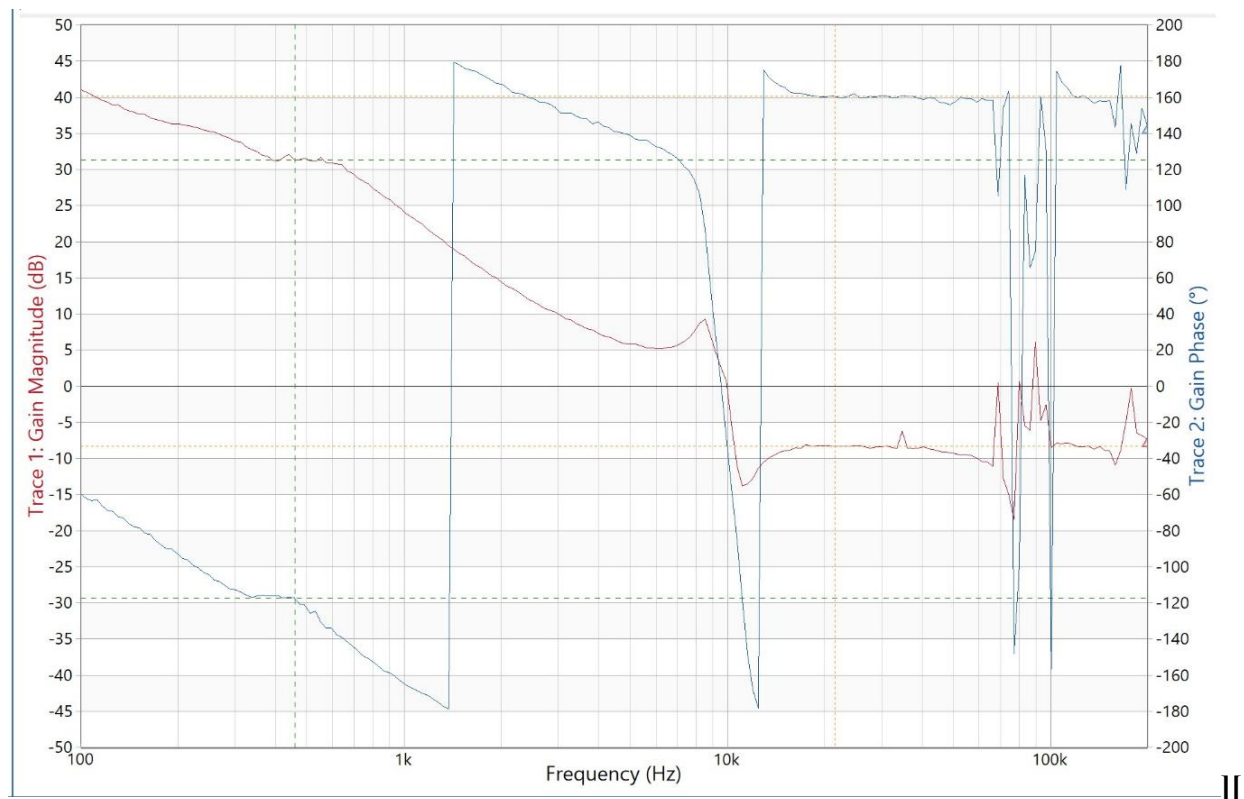



Experiment #4 Part 2
PV Power Electronics Laboratory

Completed By:
Zach Shelton & Shane McCammon

Step 1:




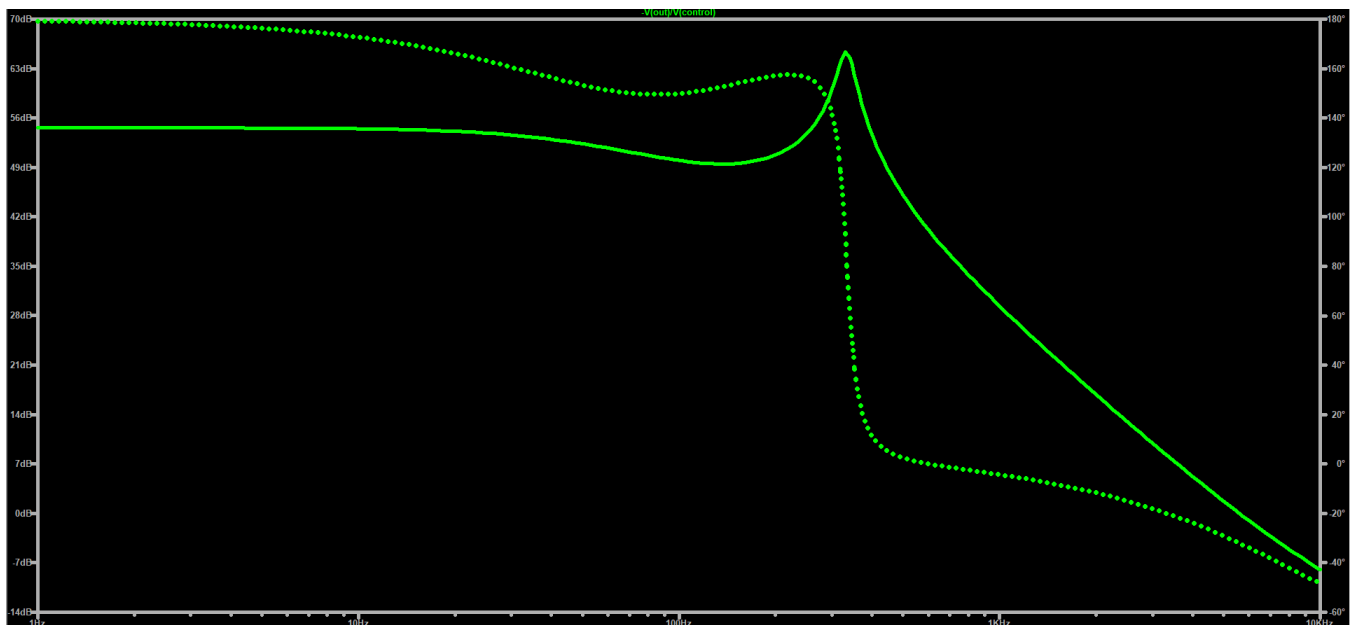Cascaded Boost Converter Open Transfer Function (Measured)



Cascaded Boost Converter Open Transfer Function (Simulated)

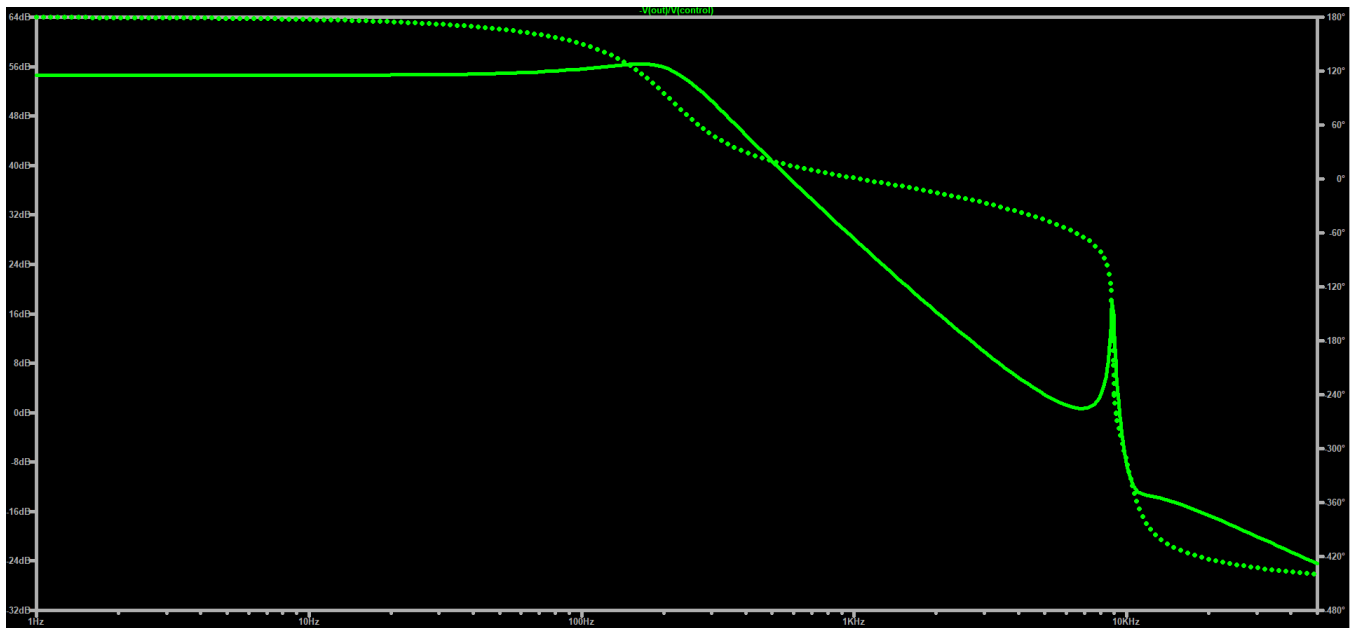
The plots differ in a lot of places, this is entirely due to the fact that the original capacitor we had in for C_2 was 1uF instead of 2200uF. Below is a simulation of what the transfer function looks like when we adjust the value of C_2 to match what was in the circuit.



Cascaded Boost Converter Transfer Function with 1uF C₂ (Simulated)

This looks much closer to what was actually measured. For future parts of this lab, the 1uF C₂ was changed to be the correct value of 2200uF.

Step 2:

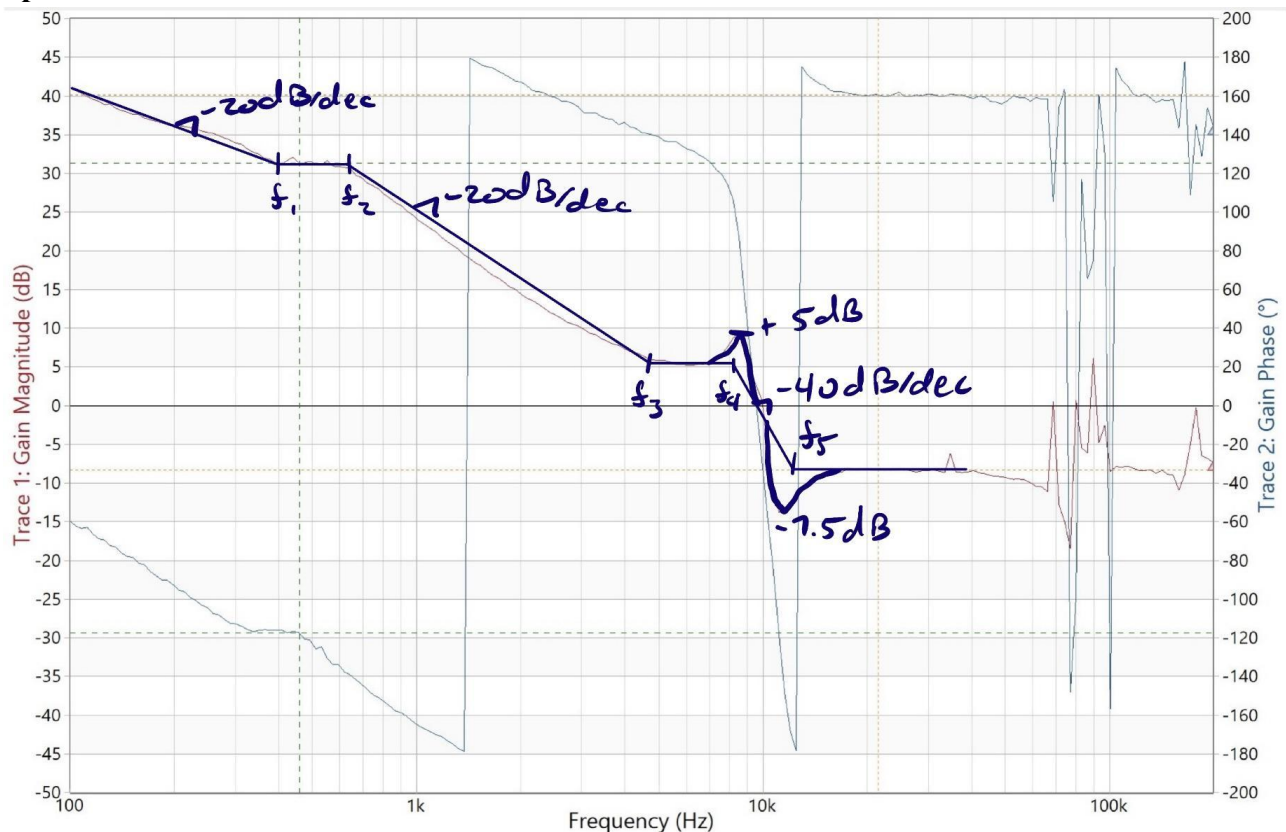

Open Loop Transfer Function Fitted Asymptotes

$$G_{vc}(s) = \frac{(1 + \frac{s}{2\pi \cdot 400})(1 + \frac{s}{2\pi \cdot 4.7k})(1 + \frac{s}{0.422 \cdot 2\pi \cdot 10k} + (\frac{s}{2\pi \cdot 10k})^2)}{(1 + \frac{s}{2\pi \cdot 100})(1 + \frac{s}{2\pi \cdot 650})(1 + \frac{s}{1.78 \cdot 2\pi \cdot 8.5k} + (\frac{s}{2\pi \cdot 8.5k})^2)}$$

$f_0 = 100$ Hz (pole)

$f_1 = 400$ Hz (zero)

$f_2 = 650$ Hz (pole)

$f_3 = 4.7$ kHz (zero)

$f_4 = 8.5$ kHz (complex pole)


$f_5 = 10$ kHz (complex zero)

$|Q_1|_{dB} = 5$ dB

$|Q_2|_{dB} = -7.5$ dB

Step 3:

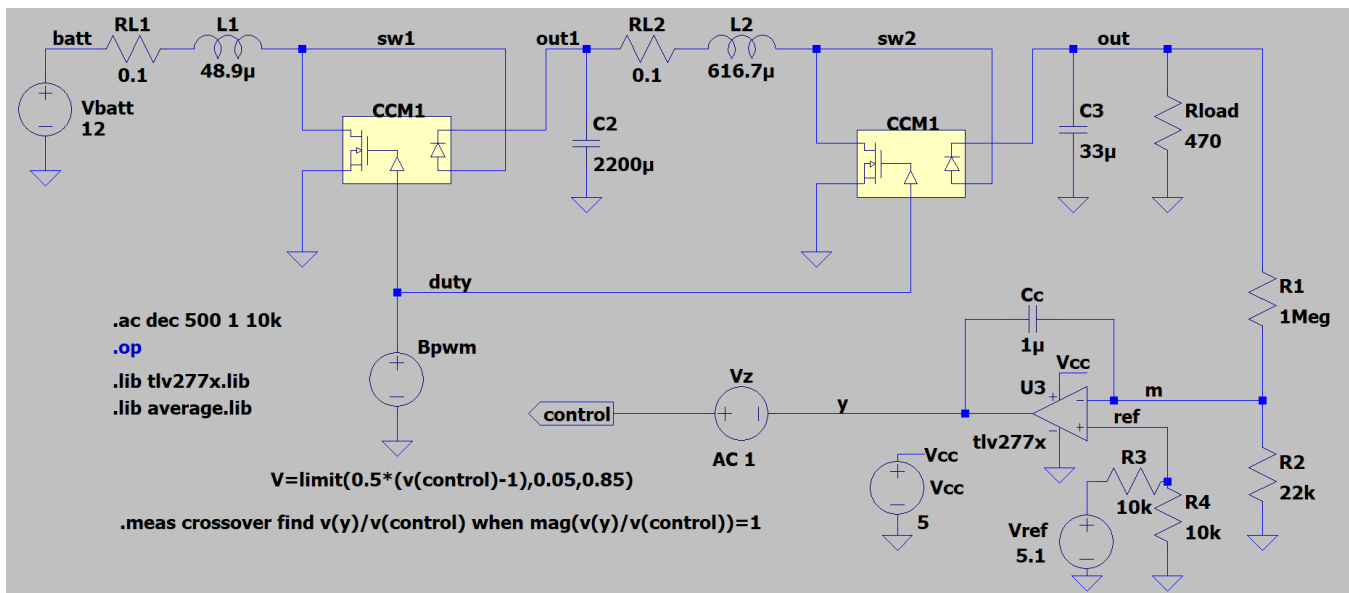The integral compensator design needed a few updates to get the stability and compensation correct. After playing around with different resistor values for the boost converter output voltage divider we settled with $R_1 = 1$ M Ω and $R_2 = 22$ k Ω . These values might need to be adjusted for the next lab, but we were satisfied with the results from these.




Detailed Circuit Diagram for Compensator Circuit

Step 4:

Switching Frequency = **92 kHz**

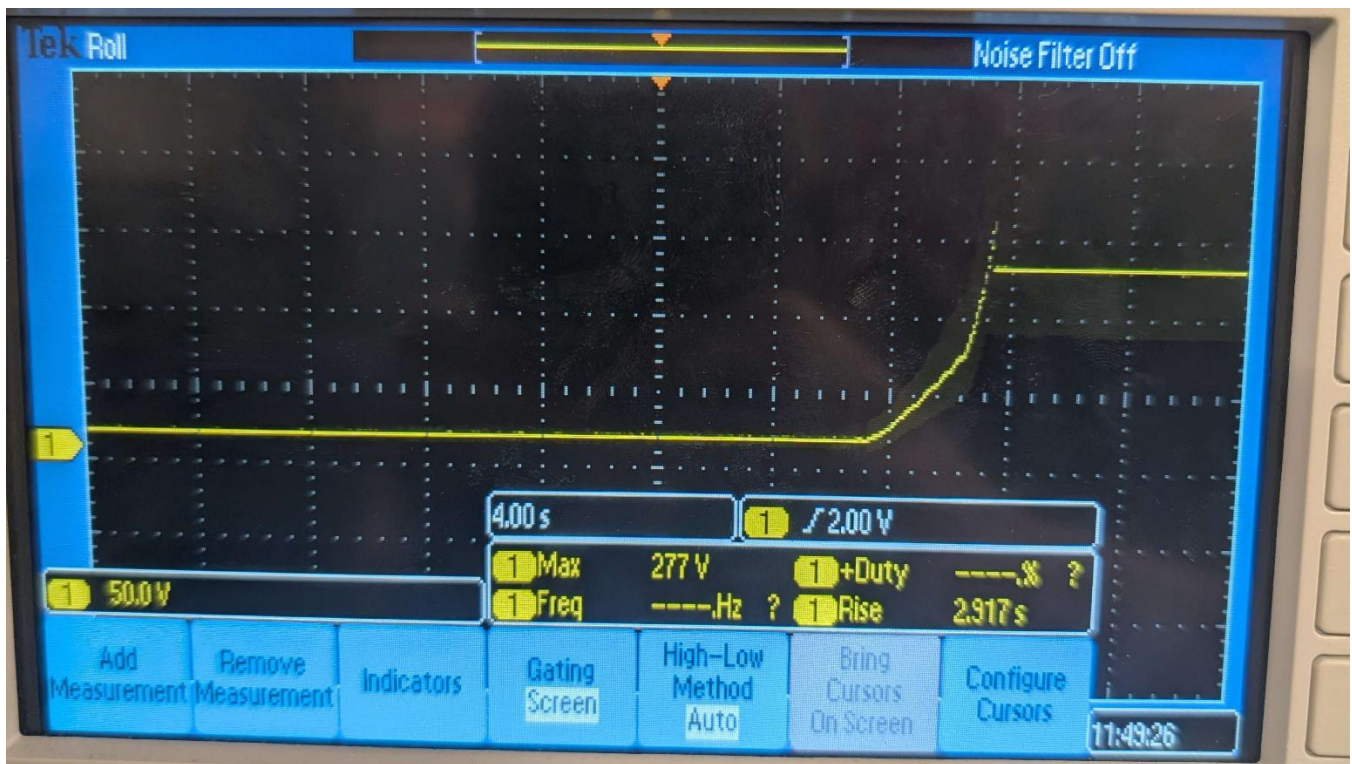
To measure the maximum duty cycle, we lowered the input voltage to drive the compensator output high. The duty cycle capped at around **88%** which is exactly what we had it set for.




Start-up Output Voltage Transient

Measured start-up time: **2.917 S**

Step 5:

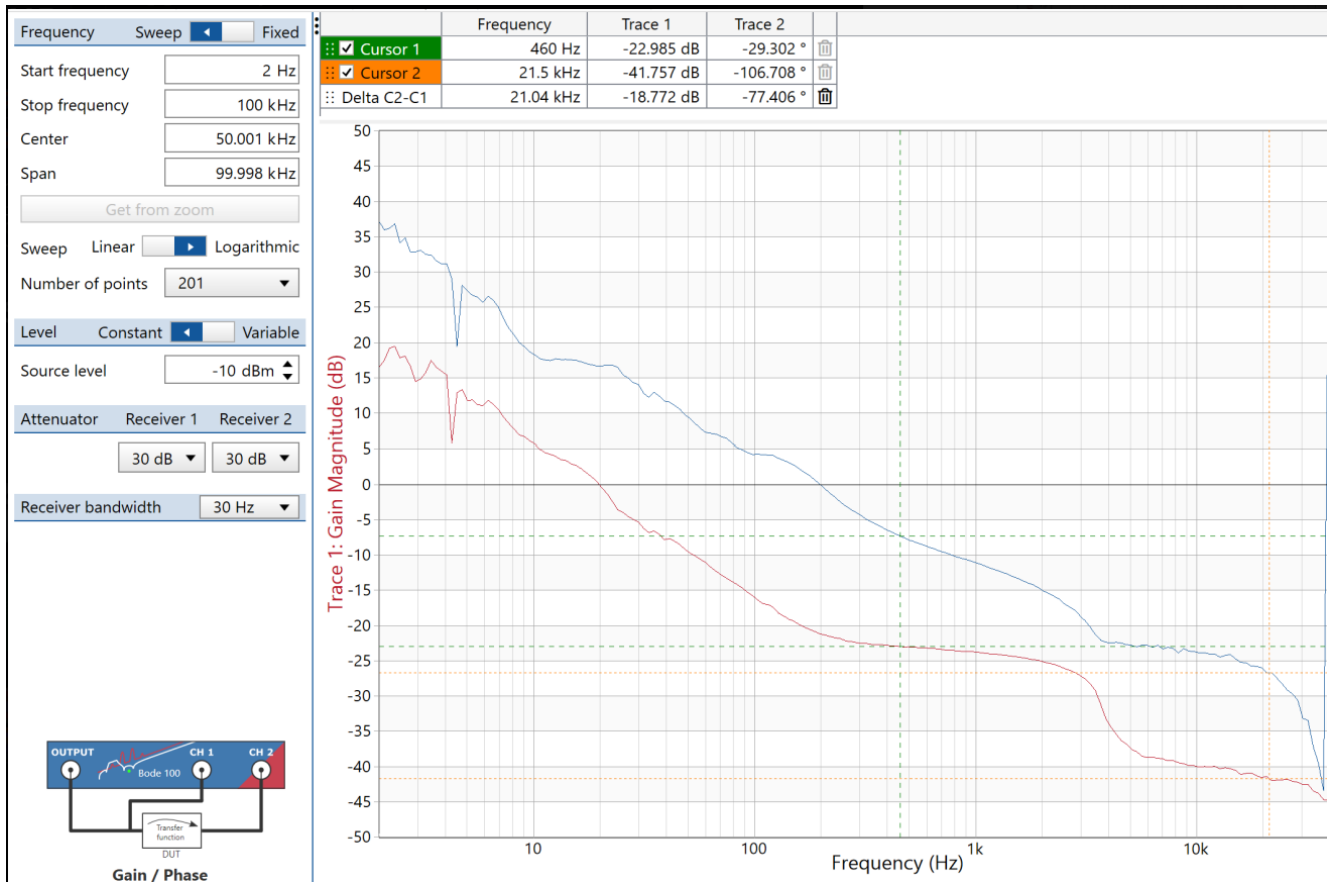

Bode100 Measured Loop Gain Bode Plot

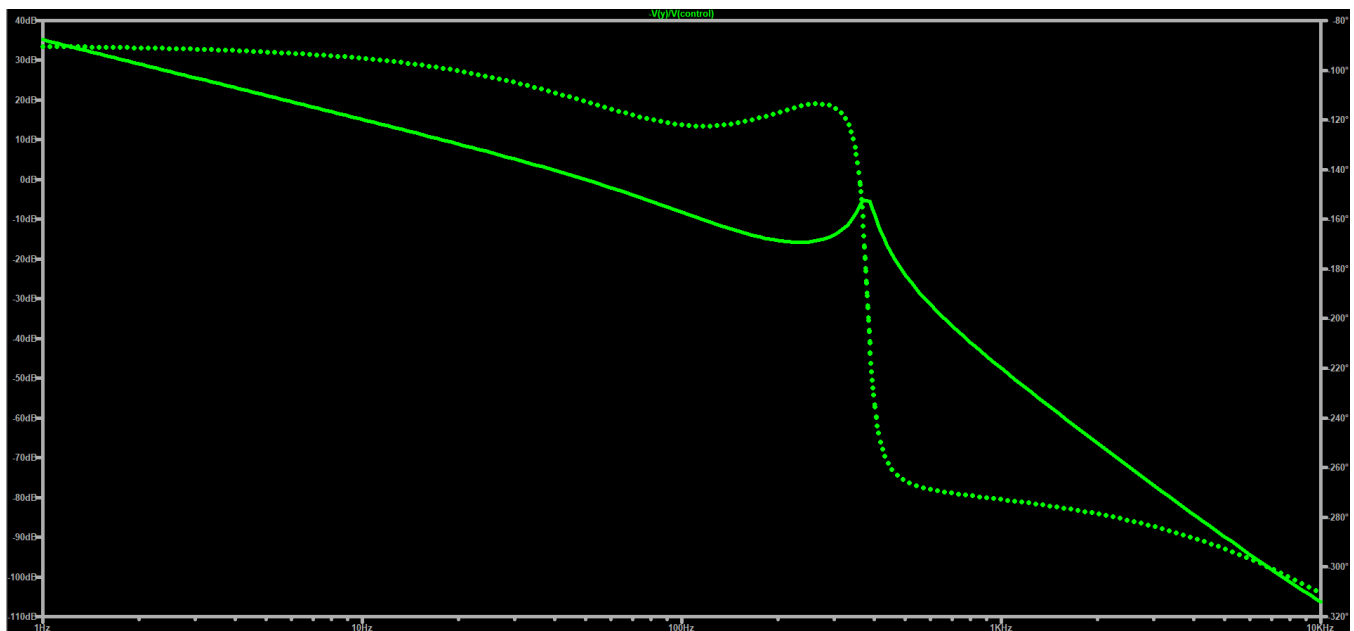

Cascaded Boost Converter Closed Transfer Function (Simulated)

Our measured crossover frequency occurred at 20 Hz with a phase margin of $(180^\circ - 16^\circ) = 164^\circ$

Our crossover frequency indicates that our system would be relatively slower with its voltage regulation although it is very stable. To improve response in our compensator we will test decreasing C_C . Our simulation showed a crossover frequency of around 20 Hz and a similar phase margin to what we measured.

Step 6:

V_{in}	I_{in}	V_{out}	I_{out}	Duty Cycle	N
11V	3.07A	127V	261mA	80%	98.16%
12V	2.66A	124V	251mA	78%	97.16%
13V	2.55A	124V	260mA	75%	97.25%
14V	2.41A	125V	265mA	72%	98.18%

Regulation:

$$127V - 124V = 3V$$

$$3V/125V = 2.4\% \text{ Regulation}$$