


Experiment #4 Part 1  
PV Power Electronics Laboratory

Completed By:  
Zach Shelton & Shane McCammon


Step 1:

No deliverable


Step 2:

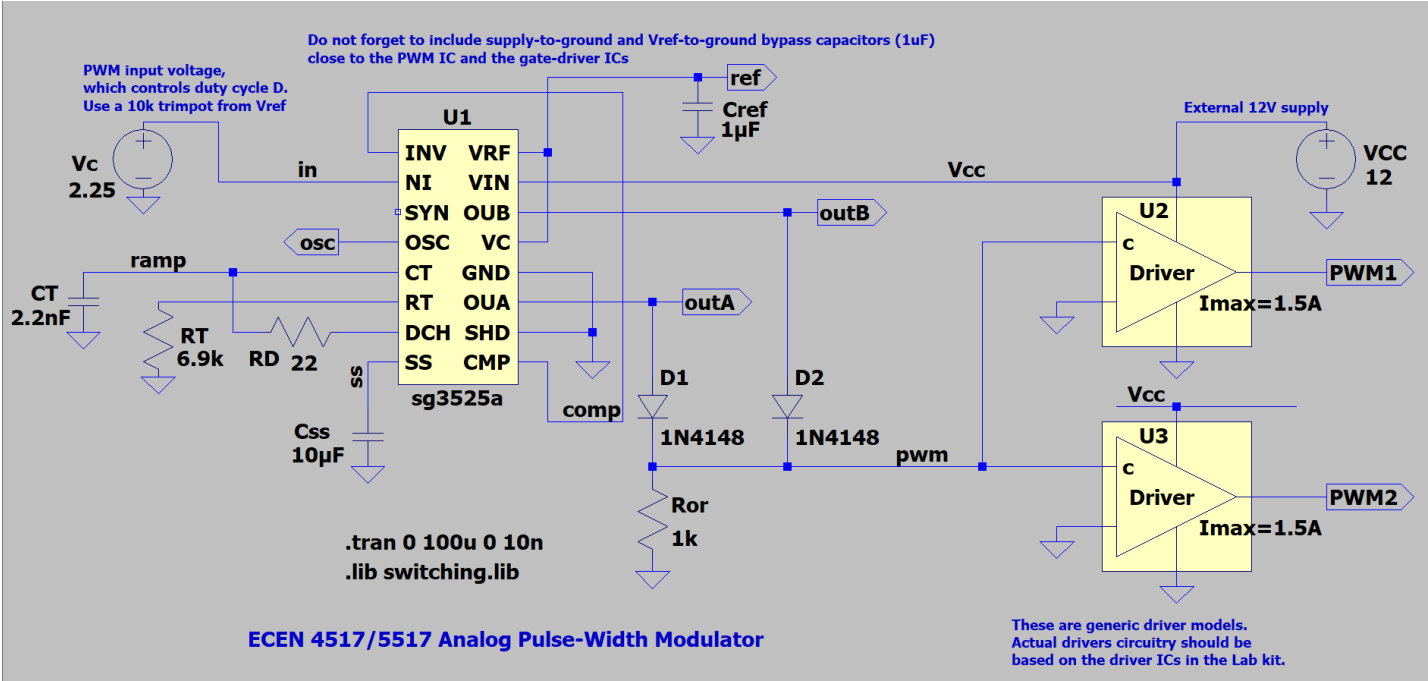


PWM Circuit Schematic

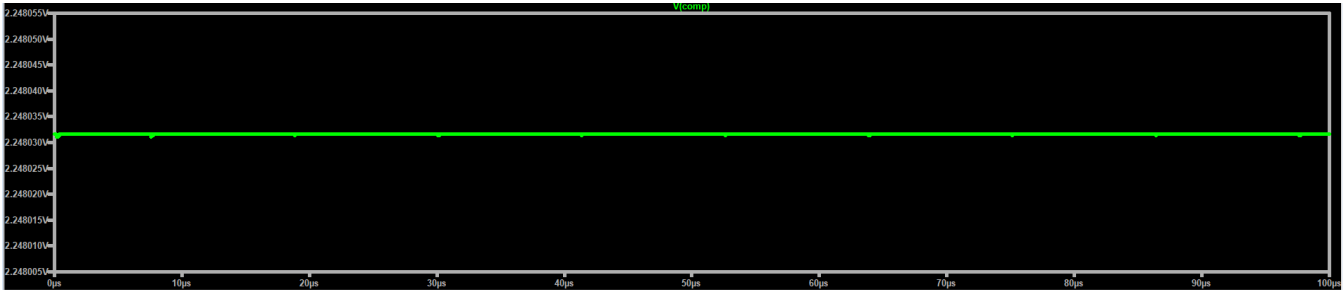


Pin 1 and 9 from Simulation (2.25V)

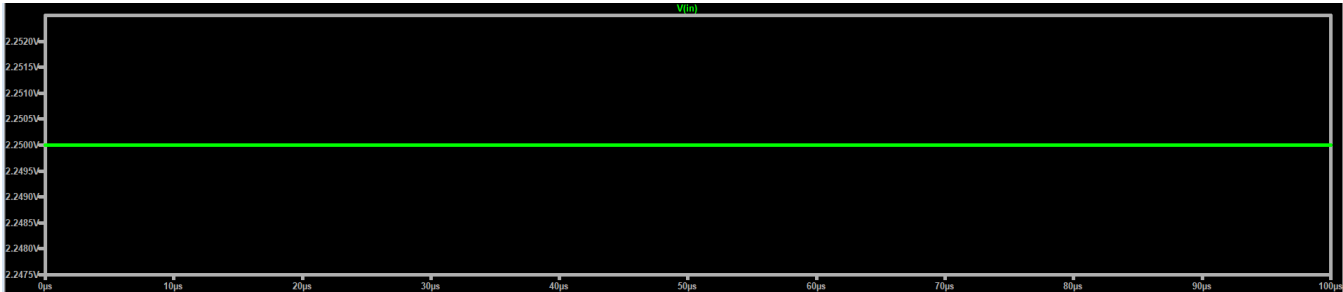


Pin 2 from Simulation (2.25V)

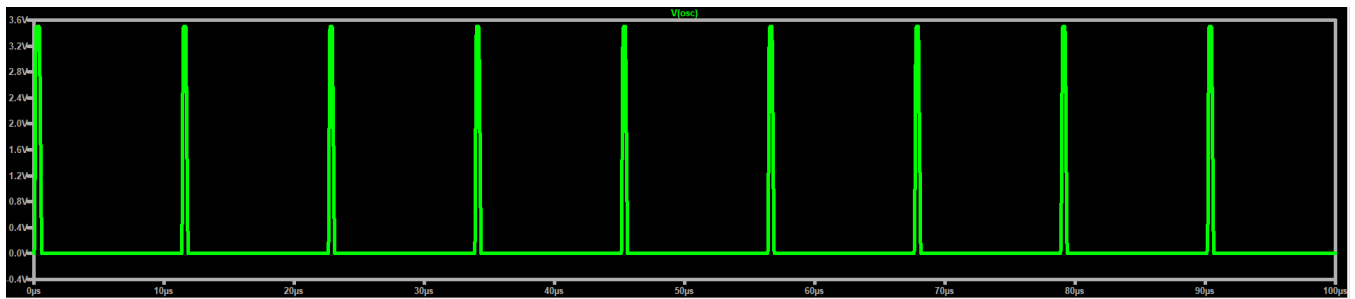


**Pin 4 from Simulation (3.6 Vpp)**

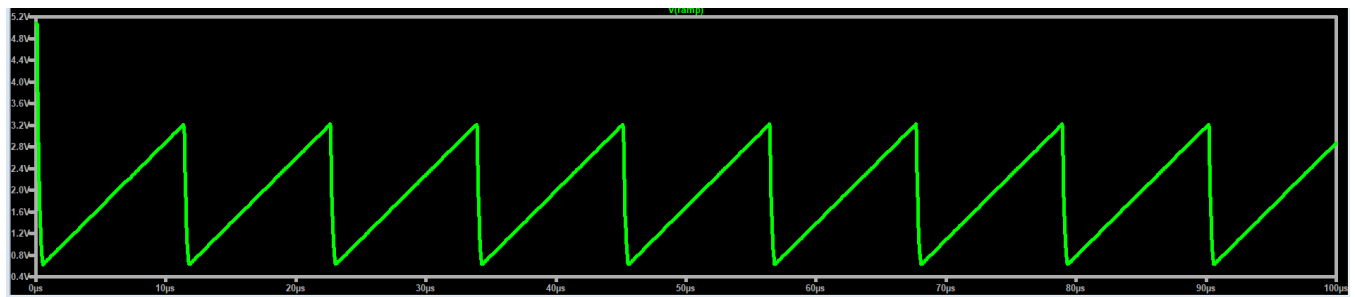


**Pin 5 from Simulation (3.2 Vpp)**

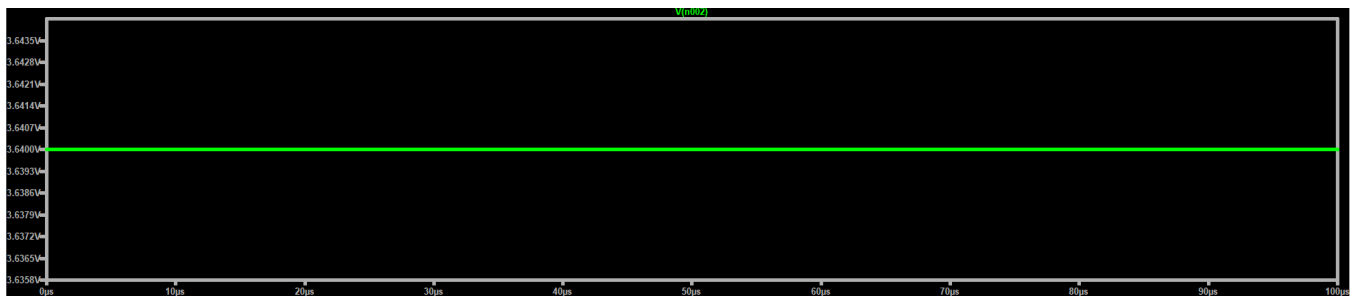


**Pin 6 from Simulation (3.64V)**

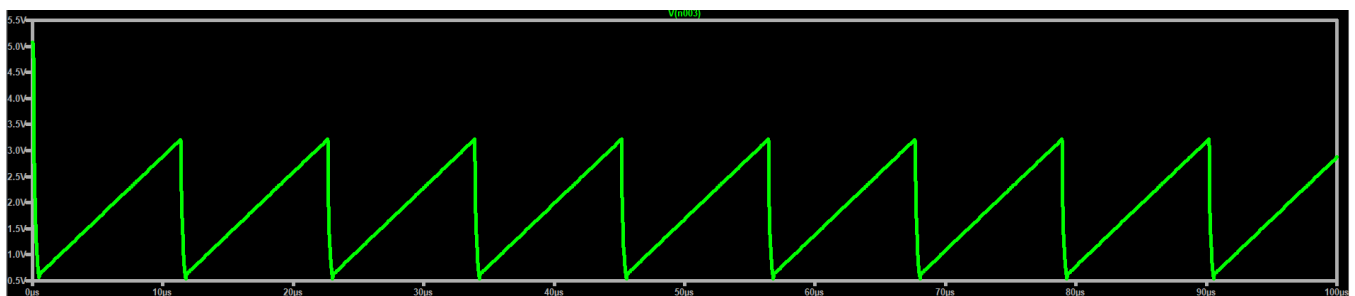


**Pin 7 from Simulation (3.2 Vpp)**

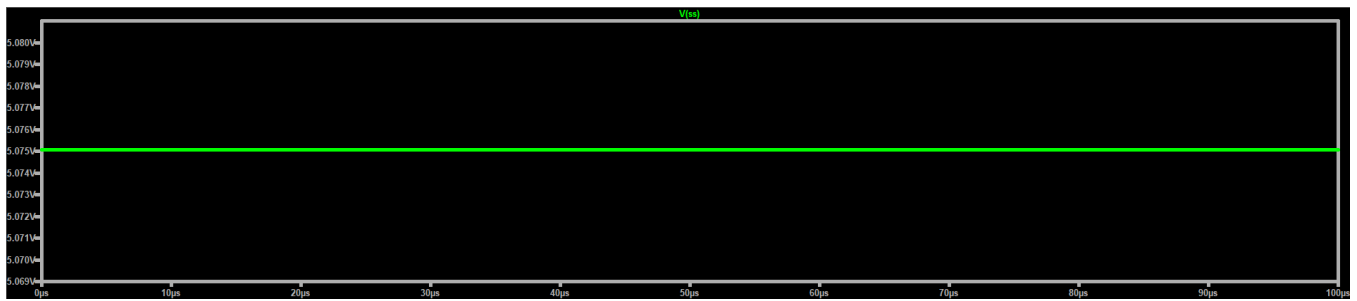


**Pin 8 from Simulation (5.075V)**

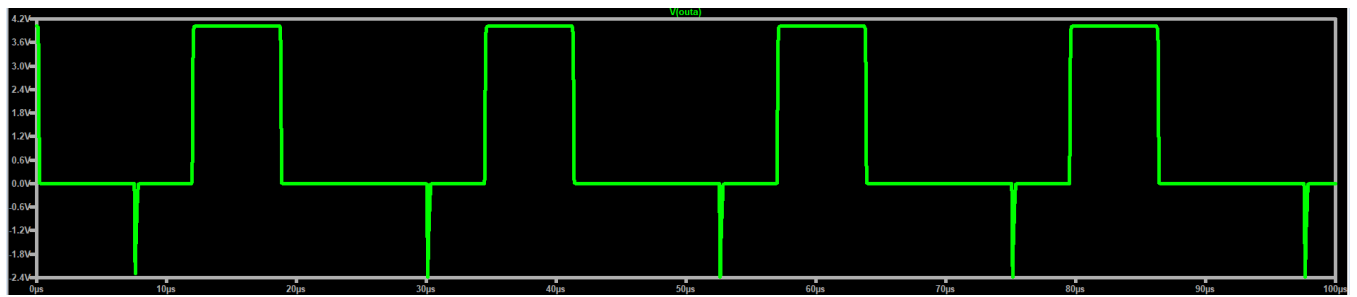

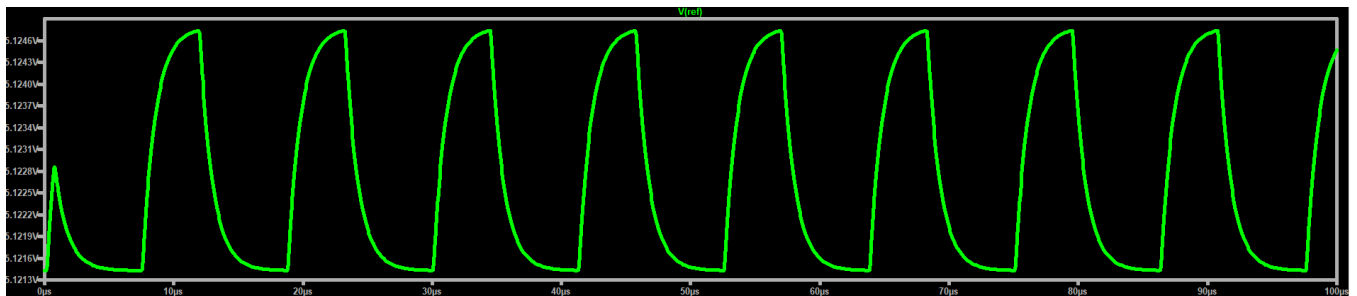
**Pin 10 from Simulation ( $V_{min} = -2.4V$ ,  $V_{max} = 4V$ ,  $D=30\%$ )**



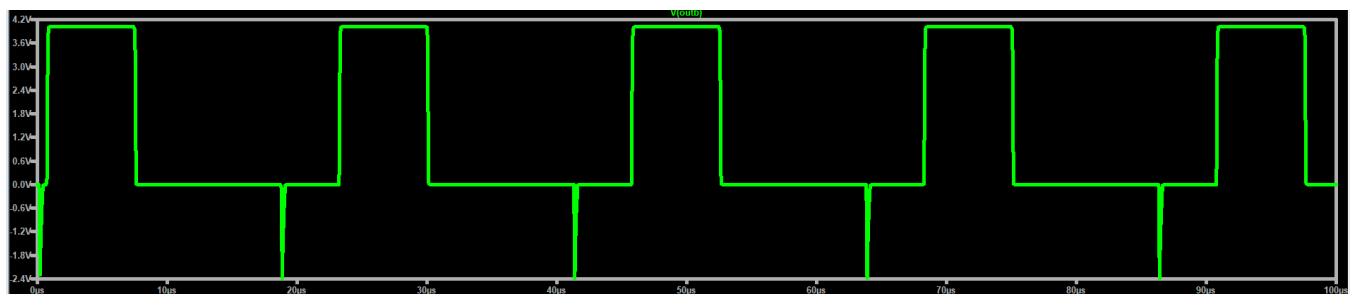
**Pin 13 and 16 from Simulation (Oscillating between 5.121V and 5.125V)**



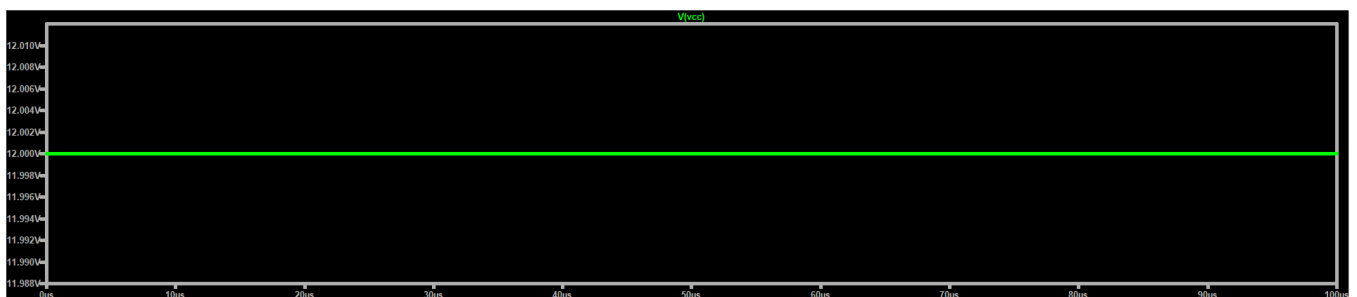**Pin 14 from Simulation ( $V_{min} = -2.4V$ ,  $V_{max} = 4V$ ,  $D=30\%$ )**




### Pin 15 from Simulation (12V)

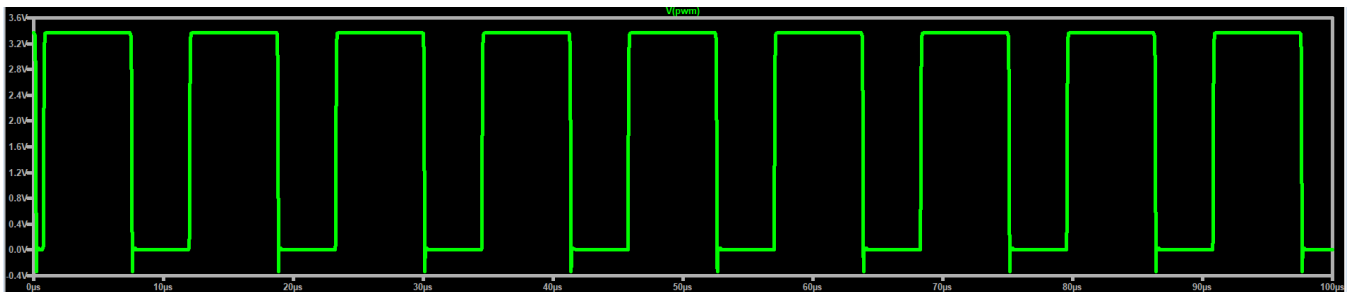


Vpwm from Simulation (Vmin = -0.4V, Vmax = 3.3V, D = 60%)

Pin 3, 10 and 12 are all ground

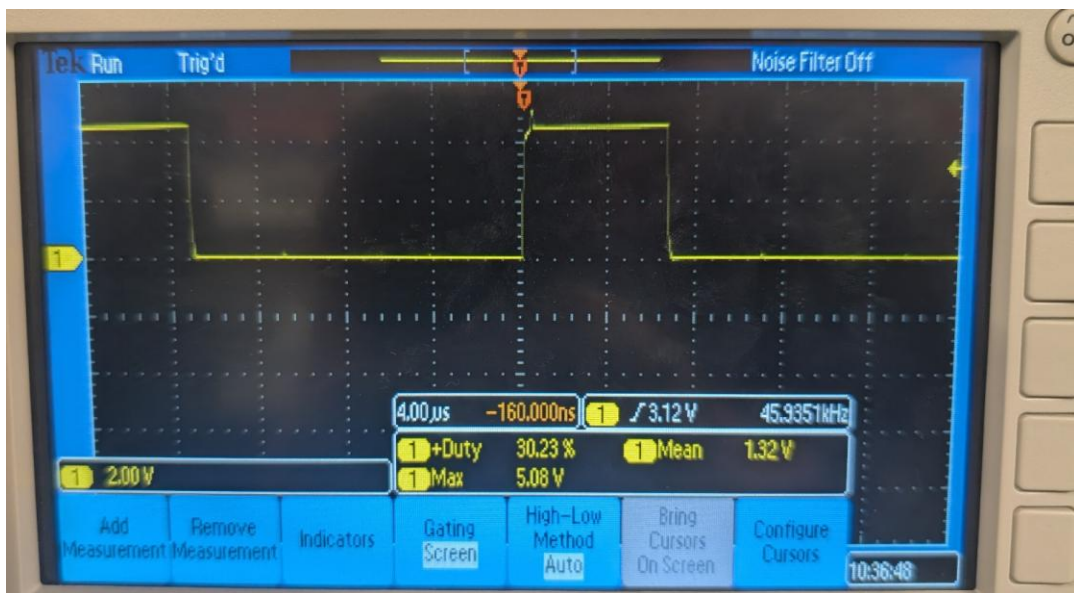

Output A (Measured)

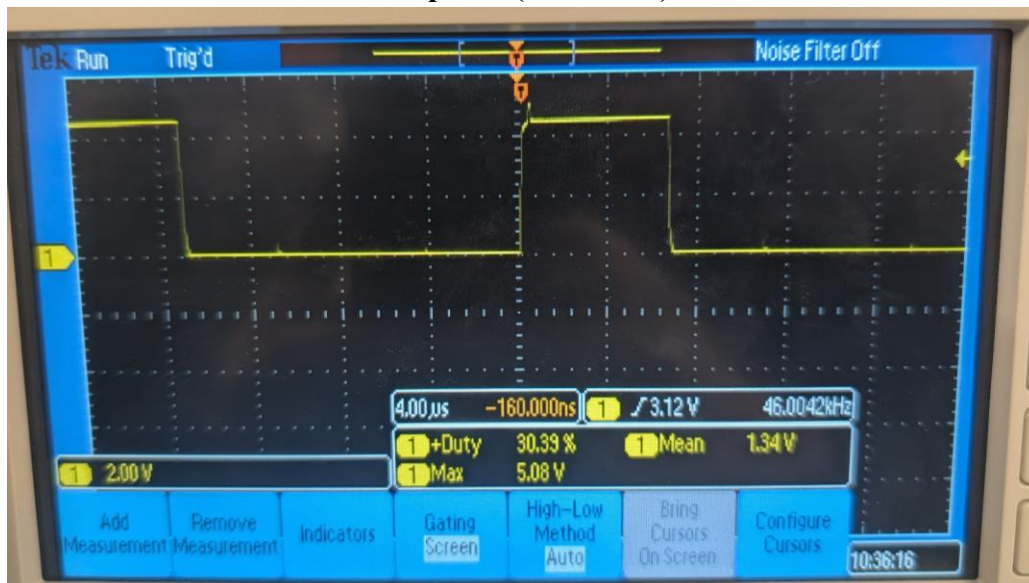


Output B (Measured)



OSC (Measured)



Ramp (Measured)

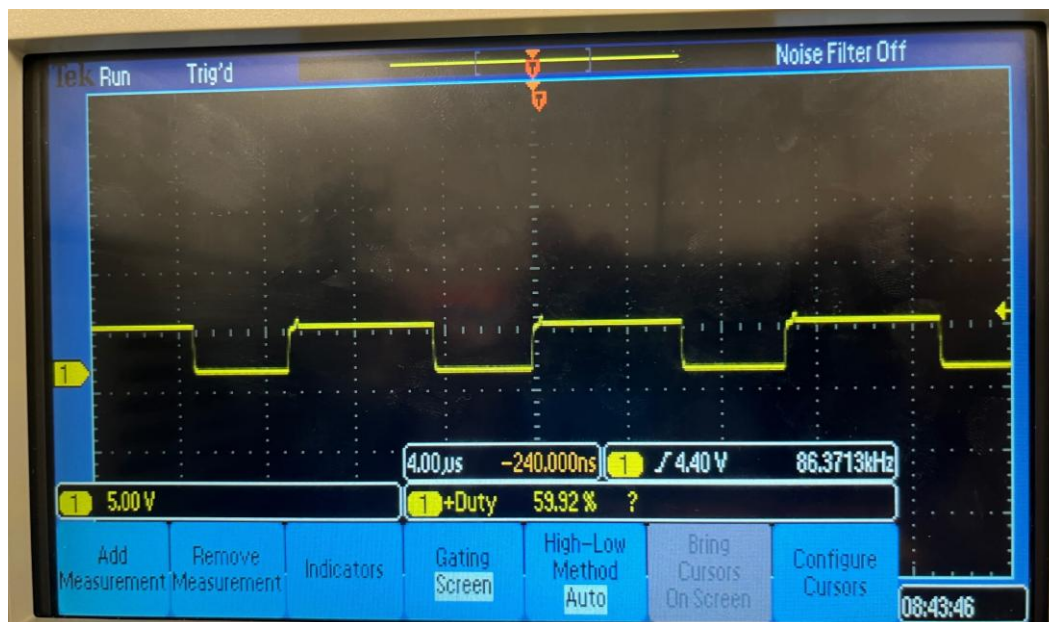

**V<sub>pwm</sub> (Measured)**

The measured results were very close to the simulated results. This shows that the PWM circuit is working how we expect it to.

**Step 3:**

Inductor Design:

$$L1: 48.6 \mu H, I_{L1} = 7.8 A, \Delta I_{L1} = 0.25 A$$

$$L2: 609 \mu H, I_{L2} = 20 A, \Delta I_{L2} = 0.25 A$$

Using PQ 26/25 core:

$$A_c = 1.18, B_{max} = 0.3, \mu_0 = 4\pi \times 10^{-7}, n = \text{turns}$$

$$L1: \frac{(48.6 \mu H)(7.8)}{(0.3)(1.18)(10^4)} = \sim 11 \text{ turns}$$

$$\text{Wire}_{L1}: \frac{(0.5)(0.503)}{11} = 22.9 \times 10^{-3} \Rightarrow \#18 \text{ gauge wire}$$

$$Gop_{L1}: \frac{\mu_0 \mu_r n^2}{L} = 3.69$$

$$L2: \frac{(609 \mu H)(20)}{(0.3)(1.18)(10^4)} = \sim 37 \text{ turns}$$

$$\text{Wire}_{L2}: \frac{(0.5)(0.503)}{37} = 6.8 \times 10^{-3} \Rightarrow \#23 \text{ gauge wire}$$

$$Gop_{L2}: \frac{\mu_0 \mu_r n^2}{L} = 3.33$$


### Measured Inductances:

L1: 49uH


L2: 610uH

Step 4:



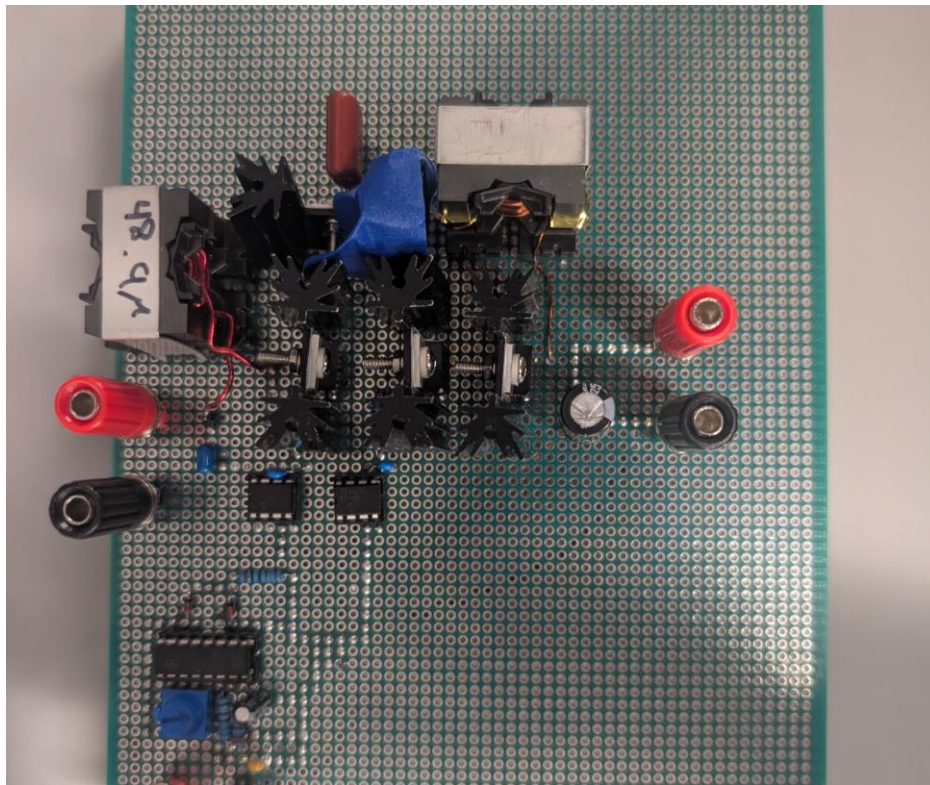

**Top Side of Boost Converter**

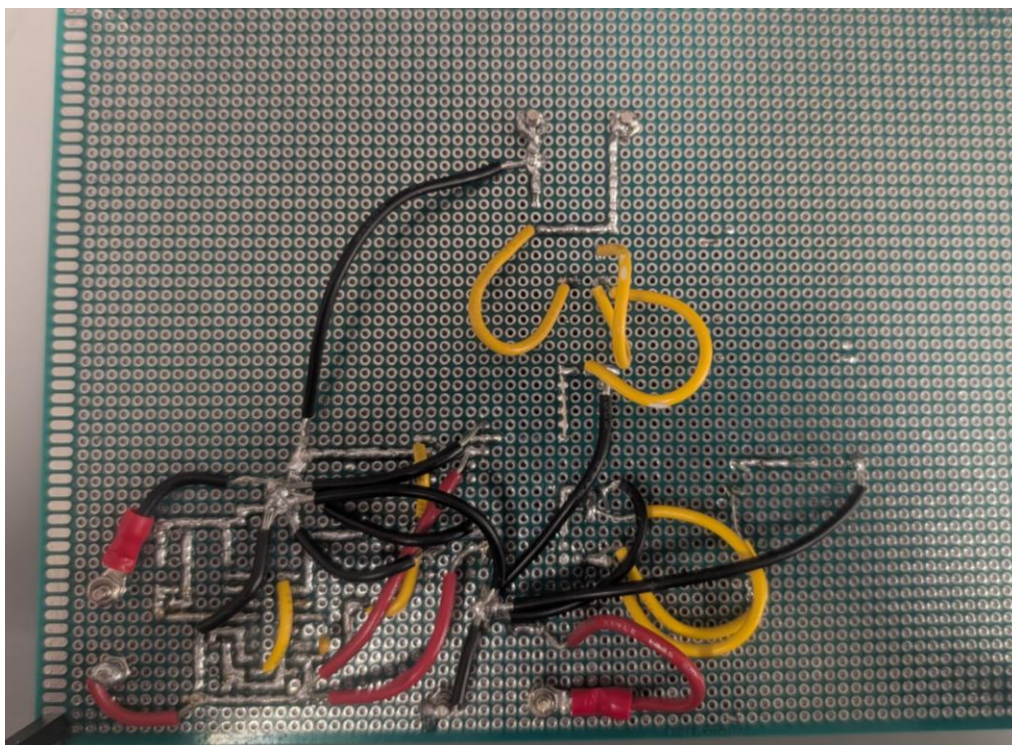

**Bottom Side of Boost Converter**

**Step 5:**

Input Voltage = 13.7V

Input Current = 7.87A


**Input Power = 107.819W**

Output Voltage = 150V

Output Current = 580mA

**Output Power = 87W**


Efficiency  $\eta$  = 80.7%

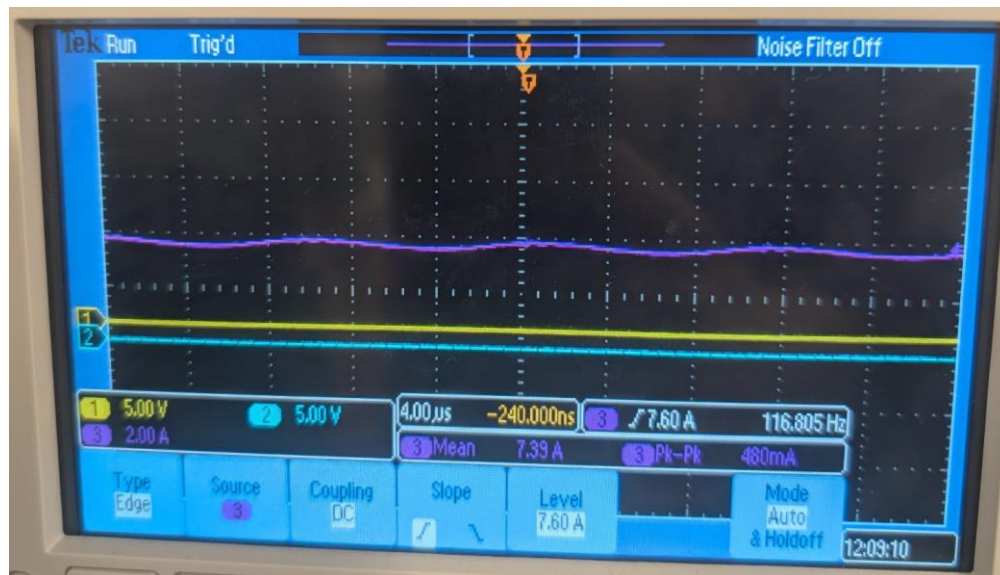

**Inductor 1 Current**

$I_{L1} = 7.4A$

$\Delta I_{L1} = 240mA$

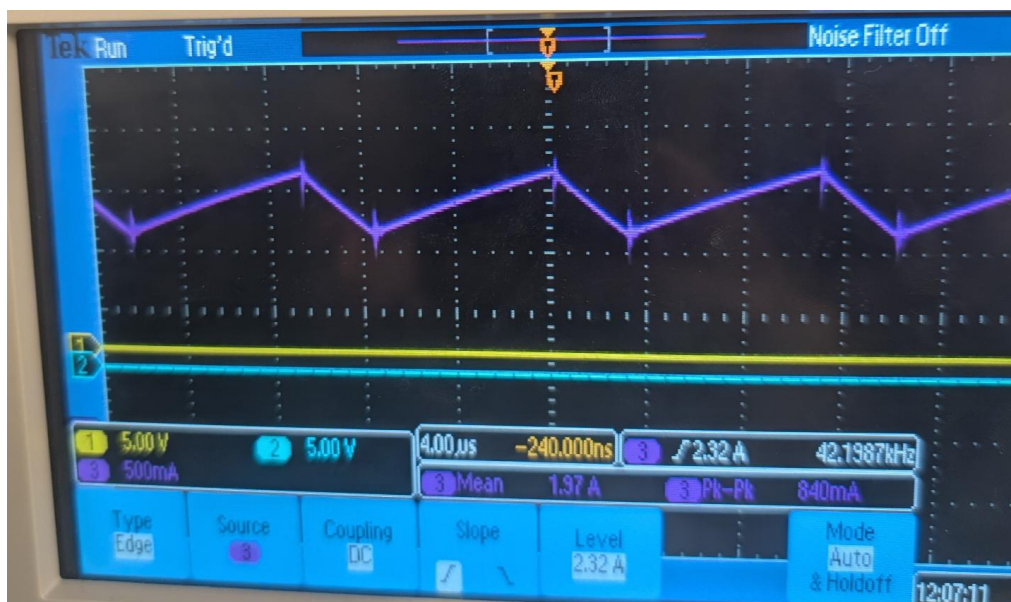




### Inductor 2 Current

$$I_{L2} = 2\text{A}$$


$$\Delta I_{L2} = 420\text{mA}$$

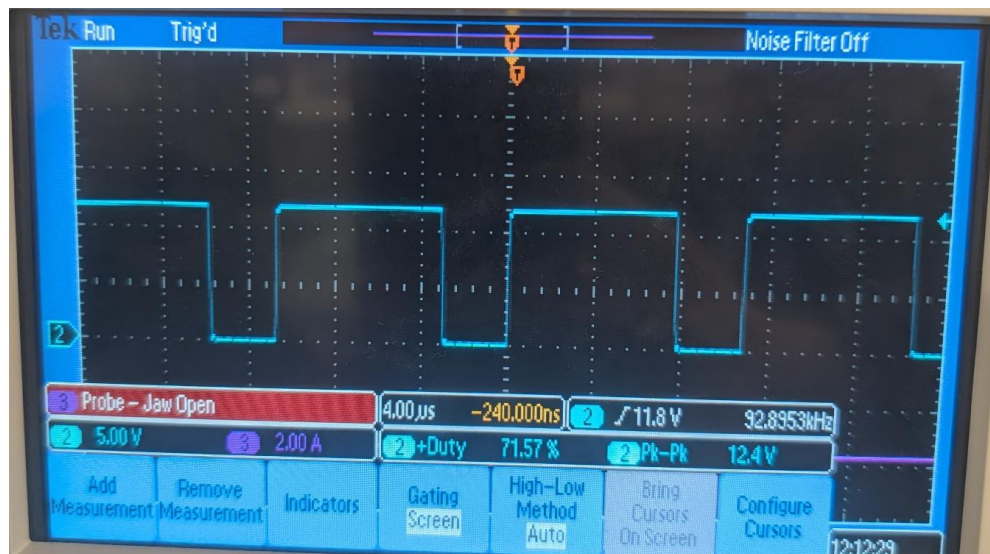

### MOSFET 1 Drain-to-Source Voltage

$$\text{Duty cycle} = 71.6\%$$

$$V_{ds1} = 12.4\text{Vpp}$$

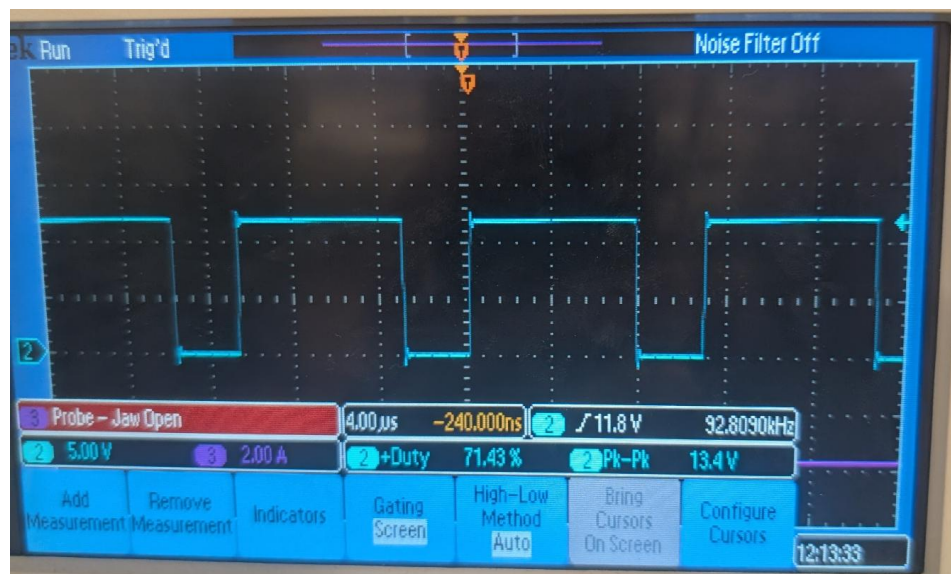

### MOSFET 2 Drain-to-Source Voltage

$$\text{Duty cycle} = 71.4\%$$

$$V_{ds2} = 13.4\text{Vpp}$$