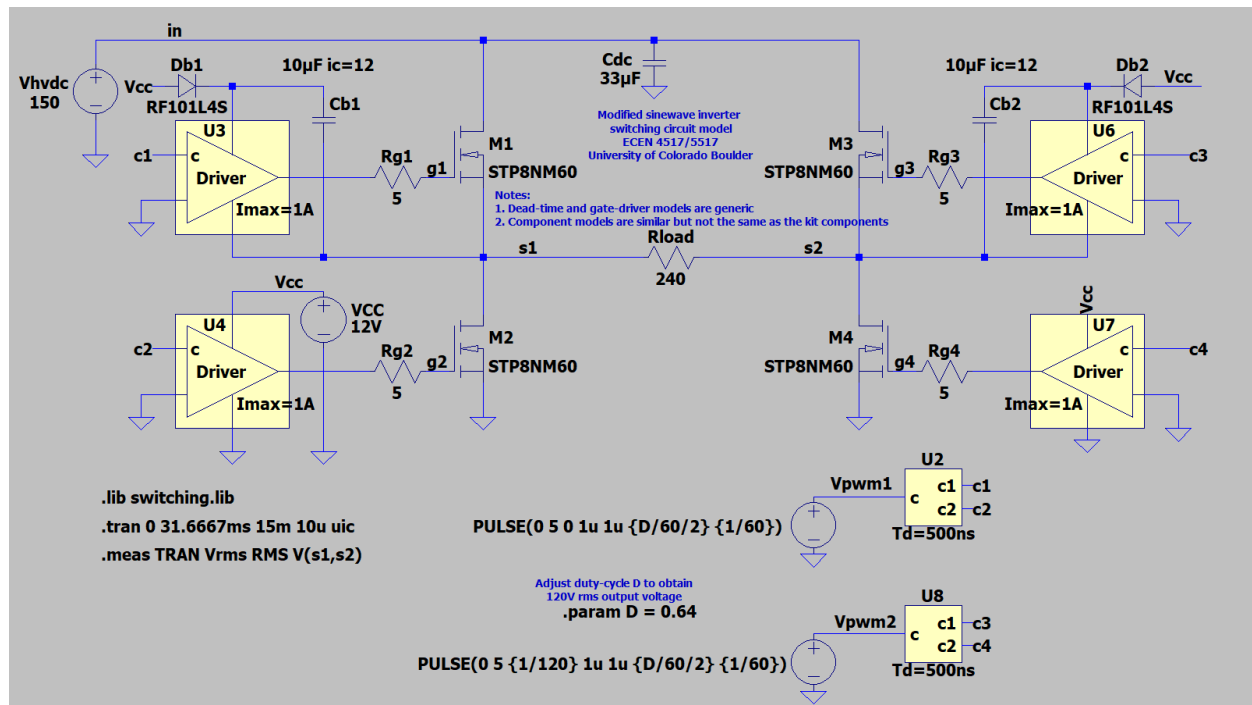


Experiment #5
PV Power Electronics Laboratory


Completed By:
Zach Shelton & Shane McCammon

Step 1:



Modified Sine Wave Schematic

Step 2:

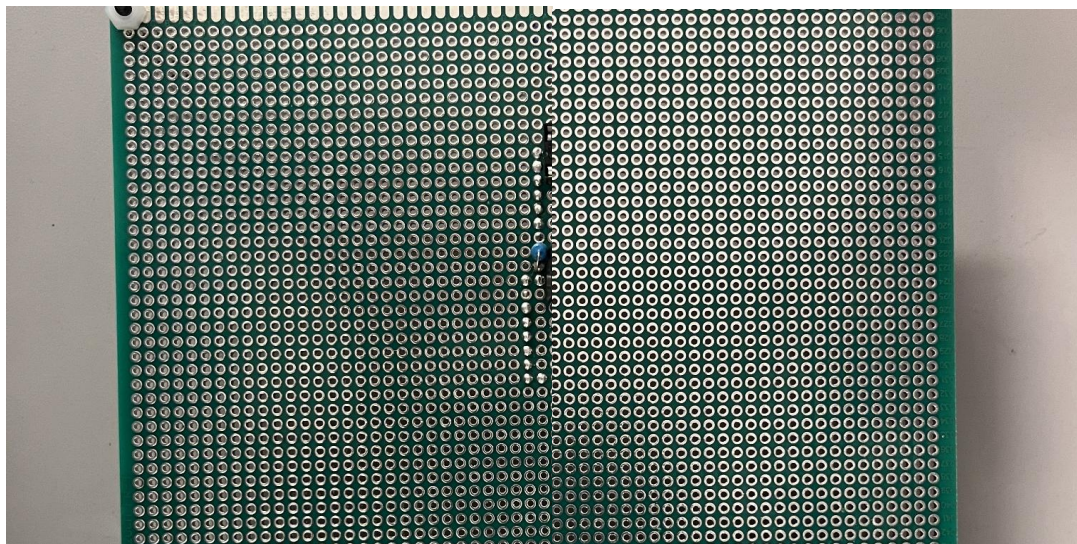

Inverter Top Side

Inverter Bottom Side

Step 3:

Modified sine-wave gate control signals:



Note that the shown frequency is 120 Hz, however, this was due to an incorrect variable value in our PWM-ADC3 code that we have fixed. The following steps will show our system operating at 60 Hz.


Step 4:

Measured Duty Cycle: 32%

Input VDC: 149.8V (It was very difficult to set the voltage source to 150VDC precisely)

Output V_{RMS} : 119V

Output I_{RMS} : 247 mA

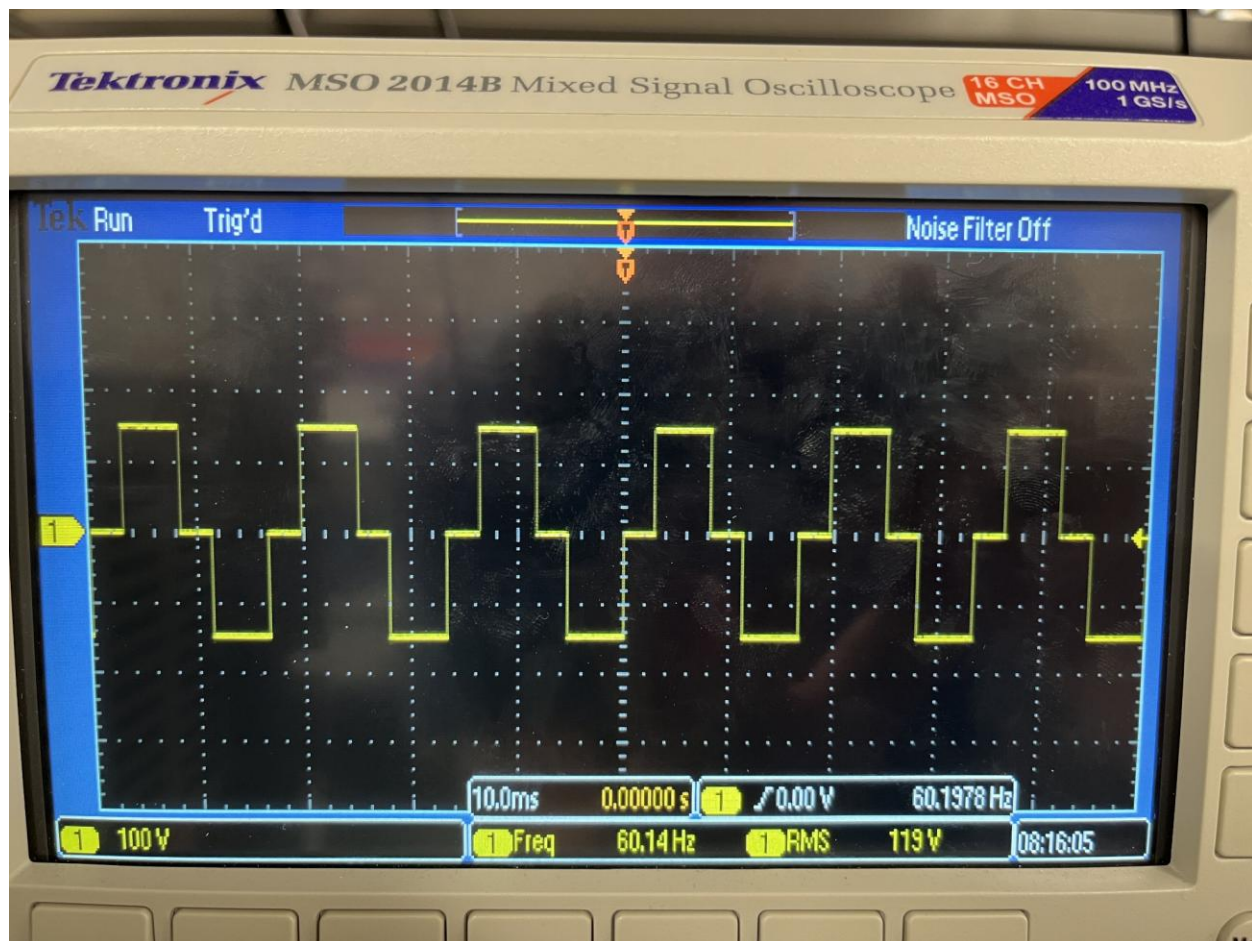

Output Voltage Waveform $120V_{RMS}$, 60Hz